

Electric circuits

Mark Scheme 3

Level	IGCSE
Subject	Physics
ExamBoard	CIE
Topic	Electricity and Magnetism
Sub-Topic	Electric circuits
Paper Type	(Extended) Theory Paper
Booklet	Mark Scheme 3

Time Allowed: 51 minutes

Score: /42

Percentage: /100

- 1 (a) (i) $I_1 = I_2 + I_3$ B1
- (ii) $I_1 = I_4$ OR same B1
- (b) (i) ($V = IR = 0.80 \times 3.0 =$) 2.4 V A1
- (ii) $I = V/R$ in any algebraic form OR 2.4 / 2 OR (b)(i) / 2
 OR any voltage divided by 2 C1
 $(I_3 = V/R = 2.4 / 2 =)$ 1.2 A A
 OR
 $I_3/I_2 = 3/2$ (C1)
 $I_3 = 3/2 \times 0.8 \text{ A} = 1.2 \text{ A}$ (A1)
- (iii) ($I_2 + I_3$ OR Current through $R = 0.8 + 1.2 = 2.0 \text{ (A)}$
 OR 6 V / 2 A used C1
 Parallel combination formula: $1/r = 1/r_1 + 1/r_2$
 OR ($r =$) $r_1 r_2 / (r_1 + r_2)$ C
 Use of formula: combined resistance = 1.2 (Ω) C
 $(R + 1.2 = 6/2 = 3.0 \Omega$ $R =$) 1.8 Ω A1
 OR
 Current through $R = 0.8 + 1.2 = 2.0 \text{ (A)}$ (
 P.D. across $R = 6.0 - 2.4$ (C1)
 $= 3.6 \text{ (V)}$ (C1)
 $R = 3.6 / 2.0 = 1.8 \Omega$ (A1)

[Total: 9]

- 2 (a) Transistor B1
- (b) Resistor / variable resistor / rheostat identified B1
 Light-dependent resistor / LDR identified B1
 Resistor or alternative in gap A; LDR in gap B B1
- (c) Thermistor / thermal resistor / heat or temperature dependent resistor identified B1
 Thermistor (or alternative name) in gap A and resistor in gap B B1

[Total: 6]

- 3 (a) (i) total $R = 320 (\Omega)$ or V per lamp = 6 (V)
 $I = (240/320 \text{ or } 6/8 =) 0.75 \text{ A}$ ecf from previous line A1 [2]
- (ii) use of $P = VI$ OR I^2R OR V^2/R C1
 4.5W ecf from (a)(i) A1 [2]
- (b) resistance of each lamp = $8 \times 1.05 = 8.4 (\Omega)$
 total $R = 240/0.9 = 266.7 (\Omega)$ OR V per lamp = $8.4 \times 0.9 = 7.56 (V)$ B1
 no. of lamps (= $266.7/8.4$) = 31.7 OR (= $240/7.56$) = 31.7 B1
 max. no. of failed lamps = 8 B1
 accept reverse logic [4]
- [Total: 8]
- 4 (a) $1/R = 1/R_1 + 1/R_2$ or $R = R_1 R_2 / (R_1 + R_2)$ or $R_1 R_2 / (R_1 + R_2)$ or use of C1
 $1/8 = 1/24 + 1/X$ OR $8 = 24R/(24 + R)$ or calculations/clear logic to eliminate C1
 wrong values A1 [3]
 12 Ω
- (b) battery and resistors correct, condone twin small circles, cell, zig-zag resistors
 resistors B1
 ammeter correct position
 ignore switches, condone breaks in circuit $\leq 1 \text{ mm}$ condone wrong symbols if clear
 two resistors in series scores 0/2 as ammeter cannot be in right place [2]
- (ii) use of $I = V/R$ in any form or V/R B1
 24 Ω resistor: $I = (6/24=) 0.25 \text{ A}$ B1
 other resistor: $I = 6/\text{his (a)}$ correctly evaluated ($6/12 = 0.5\text{A}$) accept 1 s.f. if exact
 if contradiction between answer of (a) in working and answer in answer line, base marking on answer line B1 [3]

- 5 (a) (i) $(I =) V/R$ or 230/46 C1
 5.0 A *Unit penalty applies A1
- (ii) $(P =) IV$ or V^2/R or I^2R or 230×5 or $230^2/46$ or $5^2 \times 46$
 ecf from **8(a)(i)** C1
 1100/1150/1200 W *Unit penalty applies ecf from **8(a)(i)** A1
- (b) same as **8(a)(i)** (c.a.o.) *Unit penalty applies B1 [5]
- *Apply unit penalty once onl
-
- 6 (a) (i) light-dependent resistor/LDR B1
- (ii) (in bright light) resistance of Z/LDR/circuit falls/is low B1
 current rises/is large/(starts to) flow/more p.d. across R B1
 relay (coil) magnetises/attracts/is magnet B1
 switch closes/completes second circuit B1
- (b) thermistor replaces LDR or LDR removed **and** thermistor added B1 [6]