

Electrical Quantities

Mark Scheme 9

Level	IGCSE
Subject	Physics
ExamBoard	CIE
Topic	Electricity and Magnetism
Sub-Topic	Electrical quantities
Paper Type	(Extended) Theory Paper
Booklet	Mark Scheme 9

Time Allowed: 59 minutes

Score: /49

Percentage: /100

1	(a)	1.52 kW	A1	
	(b)	(i) Each appliance is connected across 240 V supply or equivalent	B1	
		(ii) Any 2: all work on same voltage or on 240 V or mains OR all have full/stated power OR each can be on or off OR one goes off/breaks others stay on	B2	3
	(c)	(i) Current = power/voltage or 200/240 Current = 0.83 A	C1 A1	
		(ii) Energy = power x time or 1.2 x 3 Energy = 3.6 kWh or 1.3 x 10 ⁷ J	C1 A1	
		(iii) Current = 60/240 R = V/I or 240/0.25 R = 960Ω	C1 C1 A1	7
				[11]
2	(a)	I = V/R or 12/8 = 1.5 A	1 1	
	(b)	(i) 10(Ω)	1	
		(ii) 2(Ω)	1	2
	(c)	power = VI or I ² R or V ² /R = 72W	1 1	2
	(d)	(i) 12(V)	1	
		(ii) 6(V)	1	2
	(e)	(i) (resistance) less	1	
		(ii) (resistance) less	1	
				(10)
3	(a)	(i) use of charge = It or I = 90/45 current = 2 A	C1 A1	
		(ii) resistance = voltage/current or 6/2 resistance is 3 ohm	C1 A1	
		(iii) energy = Vit or Vq or 6 x 90 energy is 540 J	C1 A1	6
	(b)	idea of energy transfer is (6) J/C	C1 A1	2
				[8]

4 (a)	current = power/voltage or $150/12$ value is 12.5 A	C1 A1	2
(b) (i)	sum of currents at junction = current after junction/ $12.5 \text{ A} = 5.0 \text{ A} + I$ value is 7.5 A	C1 A1	
(ii)	power = VI or is 7.5×12 e.c.f from (i) value is 90 W	C1 A1	
(iii)	resistance = voltage/current or $12/7.5$ e.c.f. from (i) but not from (a) value is 1.6Ω	C1 A1	6
			[8]

5	a(i) steel	1	A1	
	(ii) insert bar in coil (switch on, leave, switch off)	1	B1	
	(iii) to control/measure current or stop circuit/coil overheating	1	B1	3
	b(i) $R = 12/4$ $= 3 \text{ ohms}^*$	2	C1 A1	
	(ii) $P = 12 \times 4$ $= 48 \text{ W}^*$	2	C1 A1	
	(iii) $E = 48 \times 5$ $= 240 \text{ J}^*$	2	C1 A1	6
	c(i) 5 (V)	1	A1	
	(ii) sum of p.d.'s = circuit supply p.d. above + detail eg across each component/ in closed circuit etc	2	C1 A1	3
				QT 12