

# Electrical Quantities

## Mark Scheme

<b>Level</b>	IGCSE
<b>Subject</b>	Physics
<b>Exam Board</b>	CIE
<b>Topic</b>	Electricity and Magnetism
<b>Sub-Topic</b>	Electrical Quantities
<b>Paper Type</b>	Alternative to Practical
<b>Booklet</b>	Mark Scheme 4

**Time Allowed:** 42 minutes

**Score:** /35

**Percentage:** /100

- 1 (a)  $R$  values 0.553, 1.55, 2.74, 3.74, 4.92  
 (2,3,4 or more significant figures) [1]  
 Consistent 3 or consistent 4 significant figures for final four entries [1]
- (b) Graph: [1]  
 Axes labelled and scales suitable (must include origin) [1]  
 Plots correct to  $\frac{1}{2}$  square (-1 each error or omission) [2]  
 Well judged str. line taking account of all points and reaching an axis [1]  
 Thin line [1]
- (c) Statement proportional (wtte) or as  $x$  increases,  $R$  increases [1]  
 Justification straight line through origin [1]
- (d) Clear indication of method on graph [1]  
 Correct value to  $\frac{1}{2}$  square [1]
- (e) low current/switch off between readings  
 or add (variable) resistor/lamp  
 or reduce voltage/power [1]

[Total: 12]

- 2 (a)-(c)  
 table: [1]  
 $V, A, \Omega$  [1]  
 $V$  1.8 [1]  
 $I$  0.25 [1]  
 $R$  values 7.20, 3.46(3.5) [1]  
 consistent significant figures for  $R$  (2 or more) [1]
- (d)  $y$  0.48, 0.49, 0.5 (ecf) [1]  
 2/3 significant figures and no unit [1]
- (e) correct symbols and circuit (ignore power source symbol) [1]
- (ii) voltmeter position correct [1]
- (iii) control current/voltage/resistance/speed of motor [1]

[Total: 10]

3 Table:

- (a) Units V, A,  $\Omega$  (symbol/word) [1]  
 R values 1.11, 2.19, 5.05, 9.55 [1]  
 Consistent 2 or consistent 3 sig fig for R [1]

- (b) Yes (if within 10%) No (if not) [M1]  
 Circuit 1 and circuit 2 compared [A1]

- (ii) limit current (so temperature not increased)  
 OR switch off between readings  
 OR check for zero error  
 OR Repeats  
 OR Parallax error explained  
 OR Tapping meter [1]

**[Total: 6]**

- 4 Diagram: correct symbols for ammeter and voltmeter [1]  
 correct symbols for resistor [1]  
 correct circuit arrangement [1]

Table: units V, A (symbol/word) [1]

- (c) Prediction 1 Yes – close enough (or words to that effect)  
 OR No – not close enough (or words to that effect) [1]  
 Prediction 2 Yes – approximately half (or words to that effect) [1]

Resistance at connections  
 Internal resistance of source/other sensible suggestion [1]

**[Total: 7]**