

# Energy and Voltage in circuits

## Mark Scheme 1

<b>Level</b>	IGCSE(9-1)
<b>Subject</b>	Physics
<b>Exam Board</b>	Edexcel IGCSE
<b>Module</b>	Double Award (Paper 1P)
<b>Topic</b>	Electricity
<b>Sub-Topic</b>	Energy and Voltage in circuits
<b>Booklet</b>	Mark Scheme 1

**Time Allowed:** 74 minutes

**Score:** /61

**Percentage:** /100


**Grade Boundaries:**

A*	A	B	C	D	E	U
>85%	77.5%	70%	60%	55%	50%	<50%

Question number	Answer	Notes	Marks
1 (a)	(i) Voltmeter connected in parallel with a component; component is LDR;	not in parallel with wire	2
	(ii) measure current / take current reading; divide voltage (reading) by current (reading);	accept <ul style="list-style-type: none"> <li>number of amps for current</li> <li>p.d. or number of volts for voltage</li> <li><math>R = V/I</math></li> </ul> Ignore triangle mnemonics	2
(b)	(i) B – the diameter of the hole;		1
	(ii) C – the distance from the card to the LDR;		1
	(iii) Any one of - Move ruler to cover half the hole/halfway down the hole;  Draw guide lines;  Use set square;	idea of measuring across/over the diameter at right angles to ruler Placed against ruler Ignore: move ruler nearer the hole/start from 0 on the ruler	1

Continued

Question number	Answer	Notes	Marks
1 (c) (i)	suitable scales;  axes labelled;  Plotting of points;;	Must use > half width and half height of grid units on axis labels ignore orientation of graph to nearest $\frac{1}{2}$ square, up to two marks available for this, -1 each error reject dot to dot allow a reasonably smooth curve, points should be evenly distributed about the line	4
(ii)	line of best fit;		1

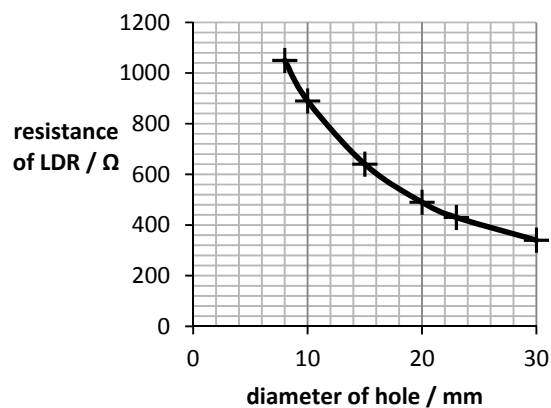

diameter / mm	resistance / $\Omega$
8	1050
10	890
15	640
20	490
23	430
30	340

(iii)	MP1	Idea of an inverse relationship;  OR  Pattern sentence linking resistance and diameter;	ignore 'negative correlation'  e.g. "the bigger the diameter, the lower the resistance"	2
	MP2	Idea of a non-linear relationship;	allow exponential decrease	

Total 14 marks

Question number	Answer	Notes	Marks
2 (a) (i)	$P = I \times V;$	accept standard symbols or in words or rearranged	1
	(ii) substitution and rearrangement; evaluation;  e.g. (I =) 110/230 (I =) 0.48 (A)	allow 0.5, 0.47826 (A) condone 0.47, 0.4782	2
(b) (i)	any suitable suggestion; e.g. carries a high(er) <u>current</u> has low(er) <u>resistance</u>	ignore references to cable overheating/melting	1
	(ii) L or live;		1
	(iii) any suitable suggestion; e.g. double insulated does not have a metal case / has a plastic case	case is not a conductor / is an insulator	1


(c)	<p>substitution into a suitable equation;</p> <p>time in correct units;</p> <p>evaluation;</p> <p>e.g.  <math>(E = I \times V \times t)</math>  <math>(E =) 0.17 \times 230 \times 55 \dots\dots\dots 1 \text{ mark}</math>  <math>(E =) 0.17 \times 230 \times 55 \times 60 \dots\dots\dots 2 \text{ marks}</math>  <math>(E =) 130\,000 \text{ (J)} \dots\dots\dots 3 \text{ marks}</math></p> <p>OR</p> <p><math>(E = P \times t)</math>  <math>(E =) 40 \times 55 \dots\dots\dots 1 \text{ mark}</math>  <math>(E =) 40 \times 55 \times 60 \dots\dots\dots 2 \text{ marks}</math>  <math>(E =) 130\,000 \text{ (J)} \dots\dots\dots 3 \text{ marks}</math></p>	<p>no mark for the equation as given in the paper  allow if <math>\times 60 / 3300</math> seen anywhere in working</p> <p>129 030 (J)  allow 131 835 for use of <math>V = 235V</math></p> <p>132 000(J)</p> <p>total marks = 9</p>	3
-----	---	--	---


Question number	Answer	Notes	Marks
3 (a) (i)	Voltmeter connected in parallel with any circuit component; Component chosen is the thermistor;	Ignore a line through the voltmeter symbol	2
(ii)	(because voltage is) a controlled variable;	Allow idea of fair test	1
(iii)	Any one of - MP1. Idea of adjustment (of current or <b>circuit</b> resistance); MP2. To control the current;		1

(b)	<p>Any three of -</p> <p><b>references to the data:</b>  MP1. (yes it works) when the temps are high, the current almost matches the temperature;  MP2. (no it's not OK) when the temps are lower, the current value does not match the temperature;  MP3. It is only right at 10 (and 100);</p> <p><b>Practicality ideas:</b>  MP4. The current cannot be <b>negative</b> when the temperature is negative;  MP5. Idea that <b>Voltage</b> will not be constant/ voltage has to be adjusted to keep it constant;</p> <p><b>line ideas</b>  MP6. Line/ graph is curved /eq;</p> <p>MP7. <b>Line/ graph</b> does not pass through the origin;</p>	<p>however expressed</p> <p>e.g. About t same from 80 °C to 100 °C;  e.g. not equal at 20mA 20 °C</p> <p>allow (graph shows that) current not <b>directly</b> proportional to temperature  allow 0,0</p>	3
-----	--	--	---

Total 7 marks

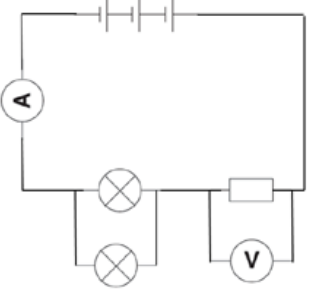

Question number	Answer	Notes	Marks
4 (a)	mark each of these independently: MP1. a <b>resistor</b> in series with the lamp only; MP2. a second lamp in parallel with the first lamp; MP3. a voltmeter that measures the voltage across the <b>resistor</b> ; MP4. an ammeter that measures the total current in the circuit;	circuit symbols used must be correct (no square voltmeter/ammeter etc.) 	4
(b) (i)	labels on axes including units; scales on axes; plotting;;	axes can be either way round must occupy >50% in each direction -1 for each error	4
(ii)	I = 0.4, V = 4.5 clearly indicated;		1

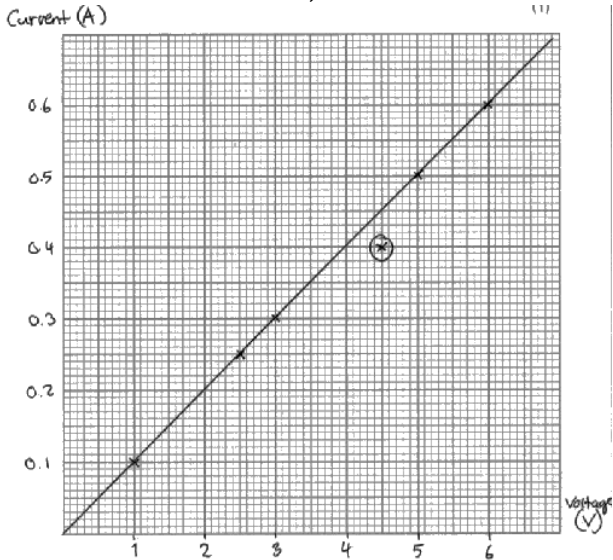(iii)	<p>Suitable line of best fit;</p> 	<table border="1"> <thead> <tr> <th>Voltage in V</th> <th>Current in A</th> </tr> </thead> <tbody> <tr> <td>1.0</td> <td>0.10</td> </tr> <tr> <td>2.5</td> <td>0.25</td> </tr> <tr> <td>3.0</td> <td>0.30</td> </tr> <tr> <td>4.5</td> <td>0.40</td> </tr> <tr> <td>5.0</td> <td>0.50</td> </tr> <tr> <td>6.0</td> <td>0.60</td> </tr> </tbody> </table>	Voltage in V	Current in A	1.0	0.10	2.5	0.25	3.0	0.30	4.5	0.40	5.0	0.50	6.0	0.60	1
Voltage in V	Current in A																
1.0	0.10																
2.5	0.25																
3.0	0.30																
4.5	0.40																
5.0	0.50																
6.0	0.60																
(iv)	voltage = current x resistance;	in words or standard symbols	1														
(v)	substitution into correct equation using any suitable pair of values taken from the graph line or table; evaluation of $R = 10 \text{ } (\Omega)$ ;	allow (0.1,1), (0.6,6) etc	2														

Total 13 marks

Question number	Answer	Notes	Marks
5 a	<p>MP1. series circuit containing lamp and some form of power supply;</p> <p>MP2. ammeter in series with lamp;</p> <p>MP3. voltmeter in parallel across lamp;</p> <p>MP4. variable resistor in series OR use of variable power supply;</p>	<p>incorrect symbols or substantial gaps =- 1 ONCE</p> <p>allow either symbol for lamp</p> <p>ignore other components e.g. switch</p>	4
b i	<p>idea that gradient changes;</p> <p>e.g.</p> <p>voltage increases more rapidly than the current</p>	<p>look for a rate change expressed in student terms</p> <p>Accept</p> <ul style="list-style-type: none"> <li>• line is curved</li> <li>• not a straight line</li> <li>• V is not proportional to I</li> </ul>	1
ii	<p>MP1. Lamp heats up;</p> <p>MP2. Greater chance of electron collisions;</p> <p>MP3. (hence) resistance increases;</p>	<p>do not award marks for a description of the shape of the graph</p>	3

(Total for question 5 = 8 marks)

Question number	Answer	Notes	Marks
6 (a) I	<p>MP1 Any circuit including <b>correct circuit symbols</b> for</p> <ul style="list-style-type: none"> <li>• battery /cell / d.c. power supply</li> <li>• ammeter</li> <li>• voltmeter ;</li> </ul> <p>ii MP2 ammeter clearly measures current through the wire; MP3 voltmeter clearly across wire;</p> <p>Idea of measuring current through the wire;</p> <p>Idea of measuring voltage across the wire;</p> <p>Idea of a range of values (of I and V); e.g. alter variable resistor OR repeat for different voltages</p>	<p>ignore other components for MP1</p> <p>allow even if voltmeter in series with ammeter allow circuit line drawn through meter allow voltmeter across a section of the test wire</p>	<p>3</p> <p>3</p>
(b) I	<p>any one of resistance changes (with temperature) ;</p> <p>ii wire gets hot <b>and</b> melts/burns/catches fire/dangerous;</p> <p>V proportional to I only at constant temperature;</p> <p>(c) Ohms Law is only true if temperature constant;</p> <p>i any one of putting the wire in a water bath ; taking the reading quickly; switching off between readings; using only small currents; voltage = current × resistance ;</p> <p>ii horizontal line above axis;</p>	<p>Reject incorrect relationship between R and <math>\theta</math></p> <p>Ignore damage to wire</p> <p>Reject insulating the wire</p> <p>Allow to return to room temperature</p> <p>Allow <math>V = I \times R</math> and rearrangements</p>	<p>1</p> <p>1</p> <p>1</p> <p>1</p>

		Total	10
--	--	-------	----