

Energy and Voltage in circuits

Mark Scheme 3

Level	IGCSE(9-1)
Subject	Physics
Exam Board	Edexcel IGCSE
Module	Double Award (Paper 1P)
Topic	Electricity
Sub-Topic	Energy and Voltage in circuits
Booklet	Mark Scheme 3

Time Allowed: 82 minutes

Score: /68

Percentage: /100

Grade Boundaries:

A*	A	B	C	D	E	U
>85%	77.5%	70%	60%	55%	50%	<50%

Question number	Answer	Notes	Marks
1 (a) (i)	voltage = current x resistance	ACCEPT equivalent rearrangement ACCEPT suitable abbreviations e.g. $V = I \times R$ REJECT $V = I \times$ REJECT equation 'triangles' alone	1
(ii)	1.2 x 4.0; 4.8 (V);		2
(iii)	12 – 4.8; 7.2 (V);	ECF on (ii)	2
(iv)	E = VI t (NO MARK) time conversion to seconds (5.0 x 60); 7.2 x 1.2 x (5.0 x 60); 2600 (J);	ECF on (iii) Allow 2592 or 2590 ALLOW 2500/2520 (J) for full marks (using 7 V) ALLOW 42 (J) or 43.2 (J) for 2 marks (using 5 mins)	3
(v)	idea of energy losses rate of energy loss = rate of energy supply (at steady temp)	NB this statement alone scores (2) as it includes idea of energy loss	2

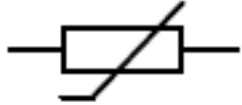
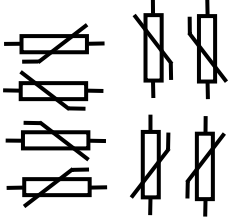
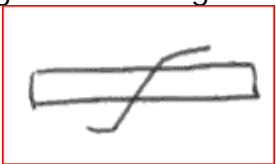
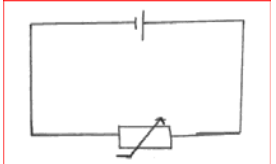

Question number	Answer	Notes	Marks
1 (b) (i)	X – series, Y – parallel	BOTH REQUIRED for the mark	1
(ii)	THREE SUITABLE, e.g. - series advantage – fewer wires; series advantage – lower resistance values; series disadvantage – one fails, circuit fails; series disadvantage – no independent control;	ALLOW REVERSE ARGUMENTS in terms of parallel circuits but do not award the same mark twice IGNORE refs to efficiency ACCEPT correct answers that link to battery voltage / current, etc	Max 3

Question number	Answer	Notes	Marks
2 (a)	any 2 of: MP1. so that lamps work independently; MP2. so that they all get mains/same voltage/230V; MP3. so that different areas/rooms can have different brightness/power/light intensities of lamps;	so that can light some rooms without all being on or off/each lamp has its own switch/if 1 lamp blows the others will still work allow no reduction in light output for main voltage allow different currents	2
(b)	D 1.38 A;		1
(c)	any 3 of: MP1. current increases over max value of fuse; MP2. fuse wire melts; MP3. cuts off current; MP4. prevents wire(s) in circuit from overheating;	allow current gets too high blows/breaks breaks circuit ignore 'stops electricity' ignore electric shocks	3


(d) (i)	power = voltage x current	allow in standard symbols or in words	1
(ii)	substitution into correct equation; evaluation; e. 0.26 X 230 60 (W)	allow 240 V for mains but not incorrect current (62.4 W) allow 59.8 (W) condone 317(.4) (W) for 1 mark	2
(iii)	answer from (d)(ii) x 180 ; evaluation; unit; e. 60 X 180 11000 joules/J	accept correct use of $E = V \times I \times t$ allow ecf from (d)(ii) mark independently allow 10800, 10764	3

2 (e) (i)	<table border="1" data-bbox="621 321 1083 646"> <thead> <tr> <th>S₁ position</th> <th>S₂ position</th> <th>lamp is lit</th> </tr> </thead> <tbody> <tr> <td>W</td> <td>X</td> <td>(yes)✓</td> </tr> <tr> <td>W</td> <td>Y</td> <td>(no) ×</td> </tr> <tr> <td>Z</td> <td>X</td> <td>(no) ×</td> </tr> <tr> <td>Z</td> <td>Y</td> <td>(yes)✓</td> </tr> </tbody> </table> <p data-bbox="495 678 737 743">any three correct; all 4 correct;;</p>	S ₁ position	S ₂ position	lamp is lit	W	X	(yes)✓	W	Y	(no) ×	Z	X	(no) ×	Z	Y	(yes)✓	<p data-bbox="1234 321 1545 418">allow 1 mark when middle two rows blank, but otherwise correct</p> <p data-bbox="1234 456 1545 553">allow 1 mark when top and bottom rows blank but otherwise correct</p>	2
S ₁ position	S ₂ position	lamp is lit																
W	X	(yes)✓																
W	Y	(no) ×																
Z	X	(no) ×																
Z	Y	(yes)✓																
(ii)	<p data-bbox="495 805 1062 1036">any sensible suggestion of 2 way switching; e. on a corridor on stairs basement/cellar bedroom/kitchen light room with 2 doorways</p>	<p data-bbox="1234 805 1560 902">allow clear description of 2 switches controlling the same light</p>	1															

Total 15 marks

Question number	Answer	Notes	Marks
3 (a)	 <p>Symbol can be in any orientation, e.g.</p> 	<p>the line through the rectangle must be correct</p>  =0 <p>Ignore the size Ignore the rest of the circuit</p>  =0 as the line through is incorrect <p>e.g.</p> <p>Allow without the connection leads</p>  =1	1
(b)	<p>(i) Voltage = current x resistance;</p> <p>(ii) Convert milliamps to amps OR kilo-ohms to ohms; Substitution into <i>correct</i> equation & rearrangement; Calculation to greater than 1SF;</p> <p>2.6 mA = 0.0026 A</p> $(R) = \frac{13.2}{0.0026}$ $= 5077 (\Omega)$	<p>Allow $V = IR$ Allow rearrangements ignore a bald 'triangle'</p> <p>'show that' question, working must be shown for full mark</p> <p>Allow 5080, 5076 (truncation) 5.080 with working is worth 2 marks 5.08 with no working is worth 1 mark</p>	1 3


Question number	Answer	Notes	Marks
3 (c)	<p>Any five of</p> <p><i>ABOUT A</i></p> <ol style="list-style-type: none"> Resistance of A decreases with temperature; For A, {largest slope / rate of change} is at lower temperature ORA {smallest slope /rate of change} is at higher temperature; A is a thermistor (ntc); <p><i>ABOUT B</i></p> <ol style="list-style-type: none"> Resistance of B increases with temperature; For B, {largest slope / rate of change} is at higher temperature(s) ORA {smallest slope /rate of change} is at lower temperature; For B, resistance is constant below 50 °C; <p><i>ABOUT BOTH</i></p> <ol style="list-style-type: none"> More results for B/ fewer results for A; stated both relationships are non-linear; Range of (temperature/resistance) values for both is similar; data comparison e.g. both have the same resistance at 80 °C; 	<p>Accept</p> <ul style="list-style-type: none"> (MP1) for A, when the temperature is low, the resistance is high, ORA (MP4) for B, when the temperature is low, the resistance is low, ORA <p>Allow component B is a ptc thermistor ORA Up to 60 °C</p> <p>Ignore: inversely proportional positive/negative correlation</p> <p>Do not take implication of MP8 when MP 1,2,4,5 is given</p>	5
		Total	10

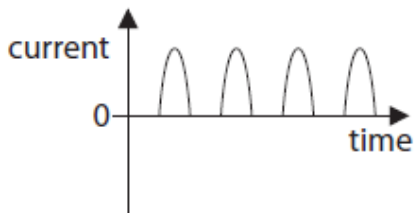Question number	Answer	Notes	Marks
4 (a) (i)	MP1. series circuit containing lamp and some form of power supply; MP2. ammeter in series (with lamp/battery); MP3. voltmeter in parallel across lamp;	correct symbols only condone cell for battery	(3)
(ii)	$V = I.R$;	accept in words rearrangements NOT the 'triangle'	(1)
(iii)	current reading from graph; calculation; unit; e.g. 1.5 (A) 4 Ω /ohms	do not accept V/A for Ω	(3)
(iv)	correct shape; correct end position/size;		(2)
(b)	 <p>D ;</p>		(1)

Total for Question 4 = 10 marks

Question number	Answer	Notes	Marks	
5 (a)	<p>CIRCUIT DIAGRAM – Correct symbols for ammeter, voltmeter and battery; Ammeter in series with cells;</p> <p>Voltmeter in parallel with wire / as shown in photograph;</p>	<p>ALLOW three separate cells in series</p> <p>ALLOW anything reasonable for the wire (e.g. straight line, variable resistor, resistor)</p>	<p>1</p> <p>1</p> <p>1</p>	
	(b) (i)	BOTH NEEDED	1	
	(ii)	<p>IGNORE references to calculating resistance, plotting graphs –</p>	5	
		<p>ANY FIVE APPROPRIATE, e.g. Connect the circuit / connect (crocodile) clip to wire; Read ammeter; Read voltmeter; For known /particular / quoted value length; measure length with a ruler; Repeat readings / average (in different places along the wire); Take readings for different lengths; Check meters for zero errors; Disconnect/switch off between readings; To avoid heating the wire;</p>		

Question Number	Answer		Marks
5 (c) (i)	Voltage = current x resistance;	ALLOW standard symbols, $V = I \times R$ ALLOW correct rearrangements DO NOT ALLOW equation given as unit symbols	1
	(ii) 6.4;	ALLOW correct answer if it follows an equation given in unit symbols IGNORE s.f. BUT must be correctly rounded from 6.4285...	1

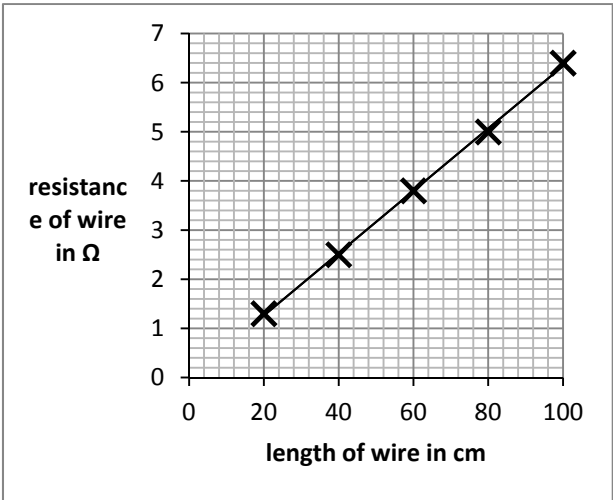Question Number	Answer		Marks										
5 (d) (i)	<p>Sample graph –</p>  <p>scale; at least half the paper axes labelled including units; Plotting; Plotting; Best fit line;</p>	<table border="1" data-bbox="1285 394 1503 602"> <tbody> <tr> <td>20</td> <td>1.3</td> </tr> <tr> <td>40</td> <td>2.5</td> </tr> <tr> <td>60</td> <td>3.8</td> </tr> <tr> <td>80</td> <td>5.0</td> </tr> <tr> <td>100</td> <td>.4)</td> </tr> </tbody> </table> <p>Points to plot</p> <p>IF AXES REVERSED, LOSE THE AXES MARK Ignore (100 cm, 6.4) ALLOW as length increases resistance increases ALLOW conclusions in terms of resistance per metre etc</p>	20	1.3	40	2.5	60	3.8	80	5.0	100	.4)	5
20	1.3												
40	2.5												
60	3.8												
80	5.0												
100	.4)												

Question Number	Answer		Marks
5 (d) (ii)	MARK (ii) and (iii) together, credit points wherever seen (directly) proportional;	IGNORE 'as length increases current decreases' / conclusions relating to current	1
	MARK tog With	ALLOW constant gradient ALLOW positive correlation	1
	(iii) any TWO of Straight line; Through (0,0); line slopes upwards; quoting appropriate values from the graph;		1
		Total	19